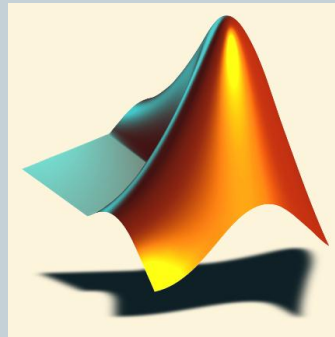


Lecture Series – 4

Solving Algebraic Equations DC Circuit Analysis

1



by

Shameer Koya

Sets of Linear Equations

2

- $x_1 + 2x_2 + 3x_3 = 366$
- $4x_1 + 5x_2 + 6x_3 = 804$
- $7x_1 + 8x_2 + 9x_3 = 351$
- In matrix form

$$\begin{bmatrix} 1 & 2 & 3 \\ 4 & 5 & 6 \\ 7 & 8 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} 366 \\ 804 \\ 351 \end{bmatrix}$$

- This is in the form

$$A * x = y$$

Hence $x = A^{-1} y$

Solving Linear Equations

3

- The problem have a solution if **rank** of A and rank of augmented matrix, ([A y]), are equal.
- $rank(A)$ rank of a matrix A is the maximum number of linearly independent row vectors of A
- $rank([A y])$
- Then test condition number of A, which should be a small number (close to 1 is better)
(the condition number associated with the linear equation $Ax = b$ gives a bound on how inaccurate the solution x will be after approximation)
- $cond(A)$
- Now the solution is
- $x = inv(A)*y$ or $x = A \setminus y$

D C Loop Analysis

4

$$\begin{aligned} Z_{11}I_1 + Z_{12} I_2 + Z_{13} I_3 + \dots & Z_{1n} I_n = \sum V_1 \\ Z_{21} I_1 + Z_{22} I_2 + Z_{23} I_3 + \dots & Z_{2n} I_n = \sum V_2 \\ Z_{n1} I_1 + Z_{n2} I_2 + Z_{n3} I_3 + \dots & Z_{nn} I_n = \sum V_n \end{aligned}$$

I_1, I_2, \dots, I_n are the unknown currents for meshes 1 through n .

$Z_{11}, Z_{22}, \dots, Z_{nn}$ are the impedance for each mesh through which individual current flows.

$Z_{ij}, j \neq i$ denote mutual impedance.

$\sum V_x$ is the algebraic sum of the voltage sources in mesh x .

D C Loop Analysis ...

5

$$[Z][I] = [V]$$

where

$$Z = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} & \dots & Z_{1n} \\ Z_{21} & Z_{22} & Z_{23} & \dots & Z_{2n} \\ Z_{31} & Z_{32} & Z_{33} & \dots & Z_{3n} \\ \dots & \dots & \dots & \dots & \dots \\ Z_{n1} & Z_{n2} & Z_{n3} & \dots & Z_{nn} \end{bmatrix}$$

$$I = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ \dots \\ I_n \end{bmatrix}$$

$$V = \begin{bmatrix} \sum V_1 \\ \sum V_2 \\ \sum V_3 \\ \dots \\ \sum V_n \end{bmatrix}$$

$$[I] = [Z]^{-1}[V]$$


In MATLAB, we can compute [I] by using the command

$$I = \text{inv}(Z) * V$$

$$I = Z \setminus V$$

Example Circuit

6

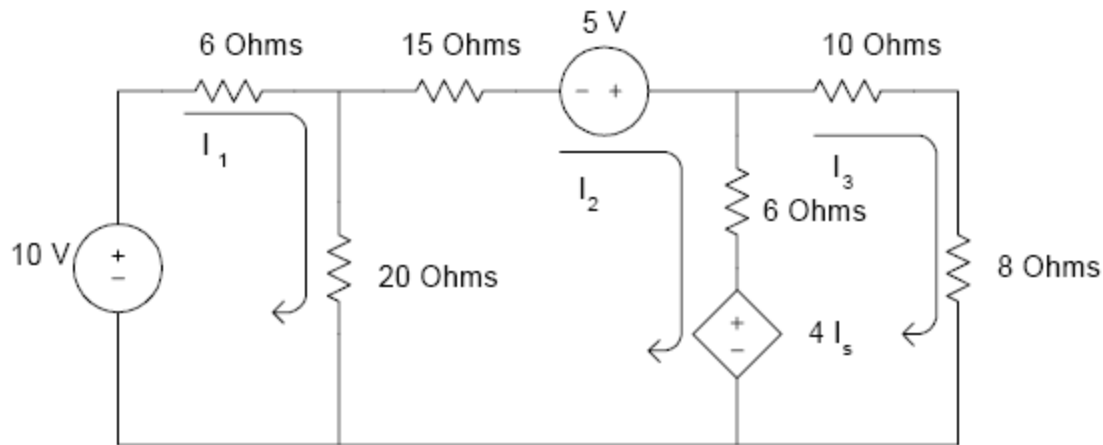

For loop 1,

$$-10 + 6I_1 + 20(I_1 - I_2) = 0$$

$$26I_1 - 20I_2 = 10$$

For loop 2,

$$15I_2 - 5 + 6(I_2 - I_3) + 4I_s + 20(I_2 - I_1) = 0$$

$$-16I_1 + 41I_2 - 6I_3 = 5$$

For loop 3,

$$10I_3 + 8I_3 - 4I_s + 6(I_3 - I_2) = 0$$

$$-4I_1 - 6I_2 + 24I_3 = 0$$

Example Circuit

7

- In matrix form:

$$\begin{bmatrix} 26 & -20 & 0 \\ -16 & 41 & -6 \\ -4 & -6 & 24 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 5 \\ 0 \end{bmatrix}$$

- Matlab Script:

- $Z = [26 \ -20 \ 0; -16 \ 41 \ -6; -4 \ -6 \ 24]$
- $V = [10; 5; 0]$
- Rank (Z)
- Rank ([Z V])
- Cond (A)
- $I = Z \backslash V$

Thanks

8

Do the exercises

Questions ??

Mid Lab: Week 8`