

Module – 3

DC MOTOR CONTROL

Lecture – 2

SPEED CONTROL OF DC MOTOR

Shameer A Koya

Outcomes

- List and describe different methods of DC motor speed control
- Explain operation of chopper drives
- Explain dynamic braking of DC motor
- Explain methods of reversing DC motor

Introduction

- Speed of a dc motor can be controlled fairly easily
- basic speed equation of a dc motor


$$n = \frac{V_t - I_a R_a}{K\Phi} \approx \frac{V_t - I_a R_a}{K I_f}$$

- there are four variables that effect speed of a dc motor i.e. V_t , I_a , R_a , and I_f
- But I_a is determined by load,
- so to control speed, V_t , R_a , and I_f are commonly used.

Speed Control


- Field current in a shunt or compound motor can be readily varied by varying external field resistance.
 - Speed is inversely proportional to field current.
 - Increasing field resistance causes a decrease in field current and therefore an increase in speed.
- Inserting a variable resistance in series with the motor armature circuit armature resistance can be changed.
 - As the series resistance is increased, the motor speed decreases
 - Used only for series motor
- Motor speed can be controlled by varying the terminal voltage
 - Very efficient and is now widely used for below the nominal speed control

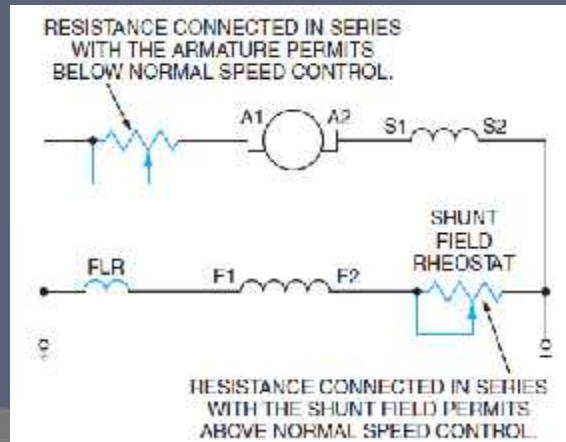- The speed corresponding to full armature voltage and full flux is known as base speed or nominal speed.
- In general **below base speed**, the flux is at maximum and speed is **controlled by armature voltage**.
- **Above base speed** the armature voltage is at or near maximum, and **flux is reduced** in order to raise the speed




DC Motor Drives – AC Drives

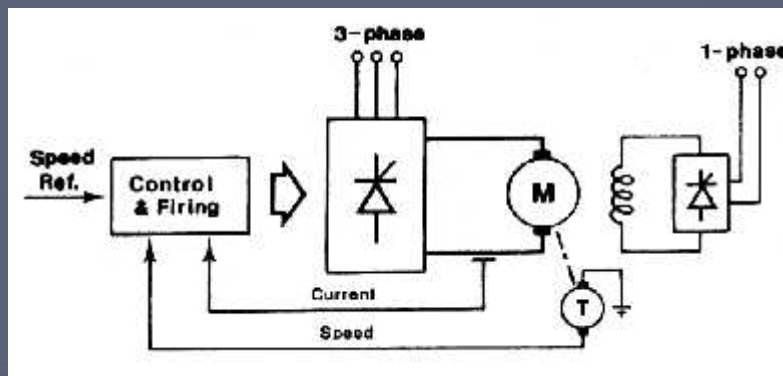- The motor armature is supplied from three-phase ac source
- A **controlled rectifier** is used to control the dc voltage to the armature
- Field is generally supplied from a single phase controlled rectifier.
- Firing of both the rectifiers is controlled by control & logic circuitry.



DC / CHOPPER DRIVES

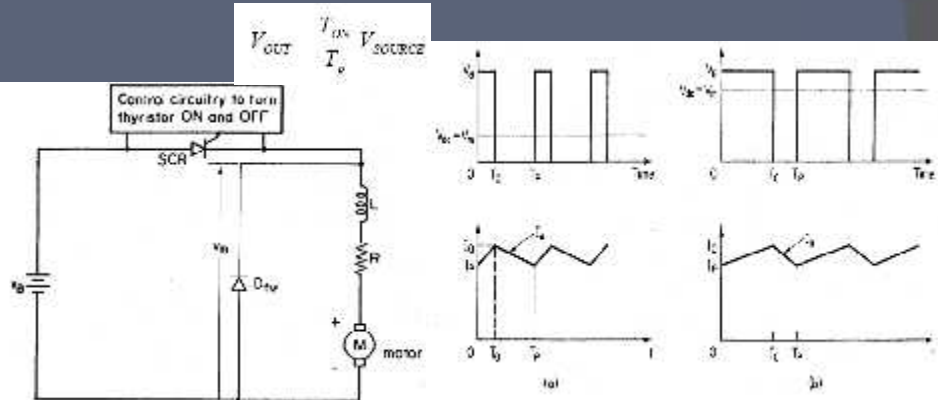
- widely used in traction application
- usually employed, when
 - source supply is dc
 - operation below base speed is important
- average voltage is varied by periodically switching the battery voltage on and off for varying intervals



DYNAMIC BRAKING


- stopping is achieved by reconnecting the motor as a generator.
- when the armature terminals are disconnected from source, a resistor is immediately connected across the armature.
- braking force is created by the current flow caused by the counter EMF and the resistor circuit.
- The mechanical energy stored in the moving parts is converted to electrical energy and dissipated across the resistor in the form of heat.
- motor cannot be stopped completely by dynamic braking alone
 - When motor slows down the generator action decreases and braking lessens.

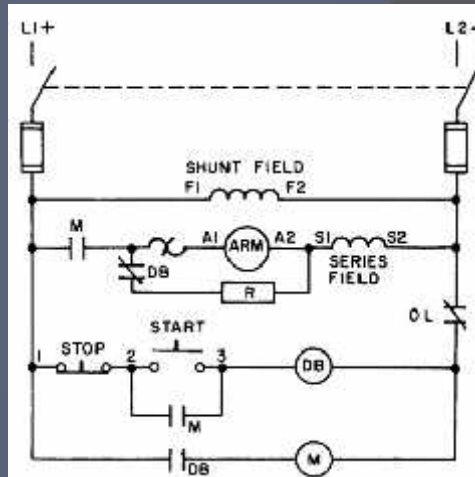- Coil DB has one normally closed and one normally open contact.
- When START button is pressed coil DB is energized and its NO contact closes, energizing coil M, which starts the motor.
- When the STOP button is pressed DB and M are de-energized
- Normally closed contact of DB completes the braking circuit through the braking resistor R.



REVERSING OF DC MOTOR

- reversing the direction of current through either the armature or the field windings, not both.
- the armature current is usually reversed.
- done by using two pairs of contacts: one set for forward, and one set for reverse.
- Care must be taken when going from forward to reverse to prevent excessive current
 - At the time of reversal, the counter EMF and the applied EMF will be of the same polarity and a high current will flow unless resistance is added

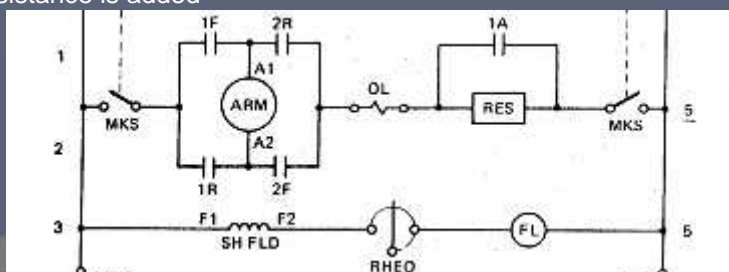

Drum controller

- drum controller is a device used to manually reverse the direction of rotation of a dc motor
- The motor can be started in the forward direction by moving the handle to the FOR position.
- To reverse the direction, the handle is moved to the REV position

