

BRAKING OF AN INDUCTION MOTOR

• There are five general methods

- Dynamic Braking
 - Energy recovered is wasted in resistor
- Regenerative Braking
 - Energy recovered is fed back into the mains
 - saves energy and money
- Plugging
 - Two phases are swapped over until motor stops.
- Mechanical Braking
 - Springs hold brake shoes against drum stopping the load from turning
- DC Injection Braking
 - When required to stop, DC is connected to two of the phases

DC INJECTION BRAKING

- Direct Current is applied to two supply lines of the motor after opening main line contactors.
- The DC produces fixed magnetic poles in the stator.
- induces a voltage in the rotor bars, which is short circuited.
- a heavy current flows in them
- This produces a magnetic field that opposes movement through the original field (a negative torque is produced)
- This action produces a braking effect on the rotor.
 - It produces less heat than the plugging
 - The braking torque is proportional to the square of the dc braking current
 - When fast braking is required, resistance should be gradually cutout from the rotor circuit to maintain the constant braking torque when the speed falls. (for wound rotor)

- Press start button, closes the M contacts and the motor start.
- Pressing Stop button, De-energize M and Energize DB.
- All M contacts will be opened and DB contact will close, thus connecting the DC from rectifier across the stator terminals.





NFF-DELAY RELAY

THR

DC Mechanical brake used for big

motors

*BR



AC mechanical brake

BAAKE

- Shoe type is preferred because they are ruggedly constructed, reliable quick acting and trouble free
- Consist of brake wheel (mounted on the motor shaft), two brake shoes (whose inner surfaces are provided with friction
- And energize the coil to remove brake

E

REVERSING OF AC MOTORS

- If the current in any two of the three-phases is interchanged, the direction of the magnetic field's rotation will be reversed.
- Any two phases are inter changed to reverse the motor.
- Can be done manually using Drum switch
- or electromagnetically using a Reversing starter



