



Semester: 2015 I

Course: EEET-221

Section No: 1

Quiz No: 1

Students ID: \_\_\_\_\_


Student Name: \_\_\_\_\_

Date: 14-09-2015

Time: 15 min

Maximum Marks: 10

Marks: \_\_\_\_\_

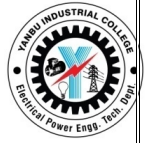

1. List Any **four** functions of an Electrical Control System

(2.0 Marks)

a.

b.

c.

d.

2. Explain about any **two** of the following.

(3.0 Marks)

Controller

Control Relay

Thermal Relay

3. Explain working of the given control circuit.

(5.0 Marks)

